

# ELECTRONIC CIRCUITS II

## UNIT 5

# Classification Of Amplifiers

## 1. According to frequency capabilities.

Amplifiers are classified as audio amplifiers , radio frequency amplifiers

- **AF Amplifier** are used to amplify the signals lying in the audio range ( i.e. 20 Hz to 20 kHz )
- **RF amplifiers** are used to amplify signals having very high frequency.

## 2. According to coupling methods.

- R-C coupled amplifiers,
- Transformer coupled amplifiers
- Direct Coupled

# Classification Of Amplifiers

## 3. According to use.

### a. Voltage amplifiers

- Amplify the input voltage, if possible with minimal current at the output.
- The power gain of the voltage amplifier is low.
- The main application is to strengthen the signal to make it less affected by noise and attenuation.
- Ideal voltage amp. have infinite input impedance & zero output impedance.

### a. Power amplifiers

- Amplify the input power, if possible with minimal change in the output voltage
- Power amp. are used in devices which require a large power across the loads.
- In multi stage amplifiers, power amplification is made in the final stages
  - ✓ Audio amplifiers and RF amplifiers use it to deliver sufficient power the load.
  - ✓ Servo motor controllers use power it to drive the motors.

## Classification Of Amplifiers


|                   | Voltage amplifiers  | Power amplifiers              |
|-------------------|---------------------|-------------------------------|
| current gain      | low                 | high                          |
| Voltage gain      | high                | low                           |
| Heat dissipation  | low                 | high                          |
| cooling mechanism | not required        | required                      |
| Transistor Size   | Small               | Large to dissipate heat       |
| Base Width        | small               | Wide to handle higher current |
| Beta              | Usually high $>100$ | Low usually $< 20$            |

# Amplifier Classes (Mode of operation)

- In small-signal amplifiers, the main factors are usually amplification linearity and magnitude of gain.
- Large-signal or power amplifiers, on the other hand, primarily provide sufficient power to an output load to drive a speaker or other power device, typically a few watts to tens of watts.
- The main features of a large-signal amplifier are the circuit's power efficiency, the maximum amount of power that the circuit is capable of handling, and the impedance matching to the output device.
- Amplifier classes represent the amount the output signal varies over one cycle of operation for a full cycle of input signal.

## **Power Amplifier Classes:**

1. **Class A:** The output signal varies for a full  $360^\circ$  of the input signal.
  - Bias at the half of the supply
2. **Class B:** provides an output signal varying over one-half the input signal cycle, or for  $180^\circ$  of signal.
  - Bias at the zero level

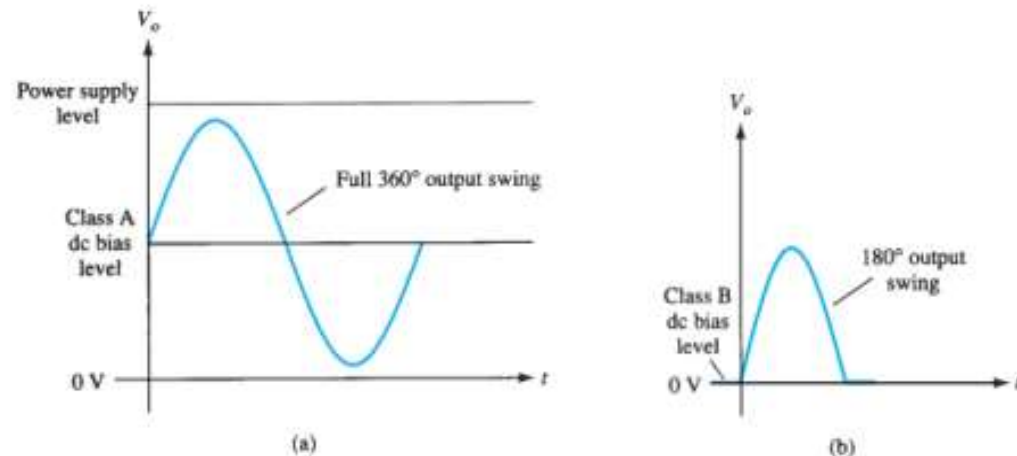

**FIG. 12.1**  
Amplifier operating classes.

# Amplifier Efficiency

## Power Amplifier Classes ...

3. **Class AB:** An amplifier may be biased at a dc level above the zero-base-current level of class B and above one-half the supply voltage level of class A.
  4. **Class C:** The output of a class C amplifier is biased for operation at less than 180° of the cycle and will operate only with a tuned (resonant) circuit, which provides a full cycle of operation for the tuned or resonant frequency.
  5. **Class D:** This operating class is a form of amplifier operation using pulse (digital) signals, which are on for a short interval and off for a longer interval.
- The **power efficiency** of an amplifier, defined as the ratio of power output to power input, improves (gets higher) going from class A to class D.


**TABLE 12.1**

*Comparison of Amplifier Classes*

|                  | A          | AB                          | Class B | C <sup>a</sup> | D                  |
|------------------|------------|-----------------------------|---------|----------------|--------------------|
| Operating cycle  | 360°       | 180° to 360°                | 180°    | Less than 180° | Pulse operation    |
| Power efficiency | 25% to 50% | Between 25% (50%) and 78.5% | 78.5%   |                | Typically over 90% |

<sup>a</sup>Class C is usually not used for delivering large amounts of power, and thus the efficiency is not given here.

# SERIES-FED CLASS A AMPLIFIER

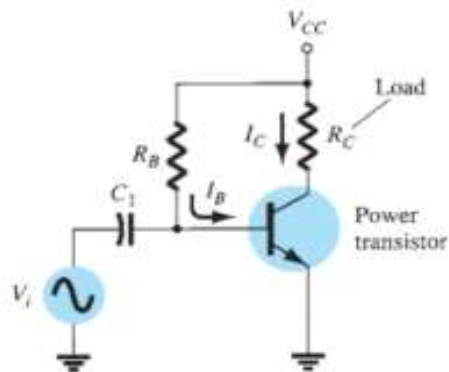

**FIG. 12.2**


Series-fed class A large-signal amplifier.

- DC Bias Operation



$$I_B = \frac{V_{CC} - 0.7 \text{ V}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

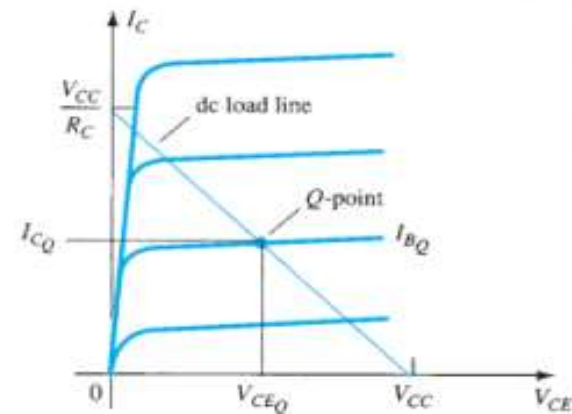

- AC Operation

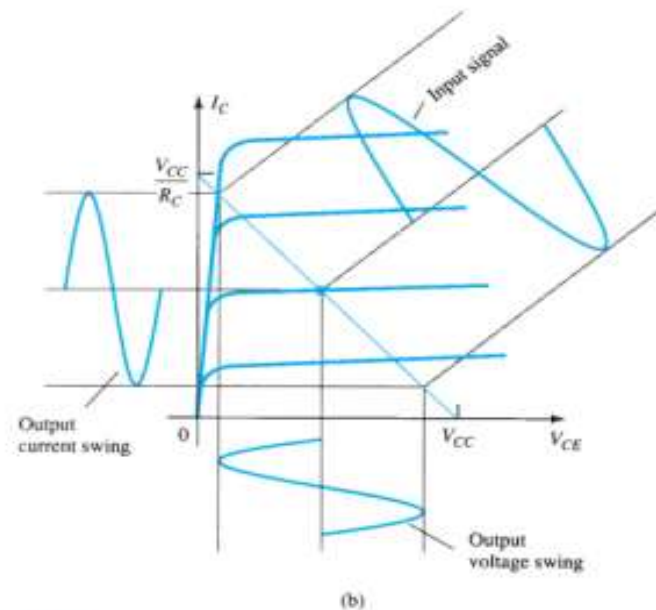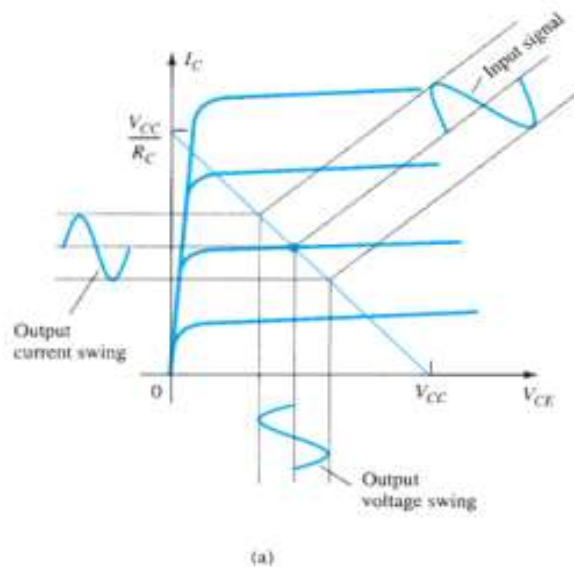

**FIG. 12.4**

Amplifier input and output signal variation.



# Power Considerations

- The power drawn from the supply is  $P_i(\text{dc}) = V_{CC}I_{CQ}$

- Output Power

$$P_o(\text{ac}) = V_{CE(\text{rms})}I_{C(\text{rms})}$$

$$P_o(\text{ac}) = I_C^2(\text{rms})R_C$$

$$P_o(\text{ac}) = \frac{V_C^2(\text{rms})}{R_C}$$

- Efficiency

$$\% \eta = \frac{P_o(\text{ac})}{P_i(\text{dc})} \times 100\%$$

- Maximum Efficiency

$$\text{maximum } V_{CE(\text{p-p})} = V_{CC}$$

$$\text{maximum } I_{C(\text{p-p})} = \frac{V_{CC}}{R_C}$$

$$\begin{aligned} \text{maximum } P_o(\text{ac}) &= \frac{V_{CC}(V_{CC}/R_C)}{8} \\ &= \frac{V_{CC}^2}{8R_C} \end{aligned}$$

$$\begin{aligned} \text{maximum } P_i(\text{dc}) &= V_{CC}(\text{maximum } I_C) = V_{CC} \frac{V_{CC}/R_C}{2} \\ &= \frac{V_{CC}^2}{2R_C} \end{aligned}$$

The maximum power input can be calculated using the dc bias current set to one-half the

$$\begin{aligned} \text{maximum } \% \eta &= \frac{\text{maximum } P_o(\text{ac})}{\text{maximum } P_i(\text{dc})} \times 100\% \\ &= \frac{V_{CC}^2/8R_C}{V_{CC}^2/2R_C} \times 100\% \\ &= 25\% \end{aligned}$$

N.B.:

$$V_{\text{RMS}} = \frac{V_p}{\sqrt{2}}$$




# THE CLASS B AND CLASS AB PUSH-PULL AMPLIFIERS

- Class B amplifier: When an amplifier is biased at cutoff so that it operates in the linear region for  $180^\circ$  of the input cycle and is in cutoff for  $180^\circ$
  - Class AB amplifiers: are biased to conduct for slightly more than  $180^\circ$
  - Both are more efficient than a class A amplifier;
- 
- A disadvantage of class B or class AB is that it is more difficult to implement the circuit in order to get a linear reproduction of the input waveform.
  - The term **push-pull** refers to a common type of class B or class AB amplifier circuit in which two transistors are used on alternating half-cycles to reproduce the input waveform at the output.
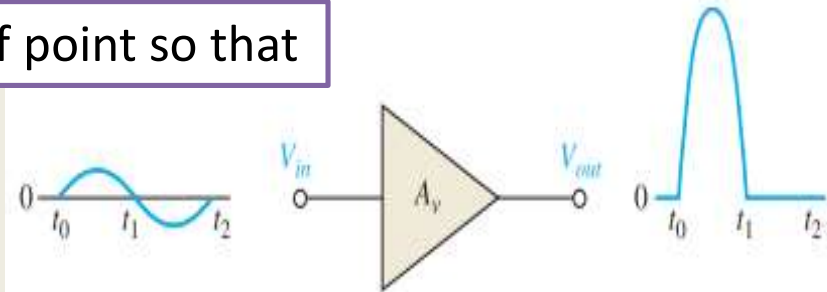
## Class B Operation


- The class B amplifier is biased at the cutoff point so that

$$I_{CQ} = 0 \text{ and } V_{CEQ} = V_{CE(\text{cutoff})}$$



- It is brought out of cutoff and operates in its linear region when the input signal drives the transistor into conduction.

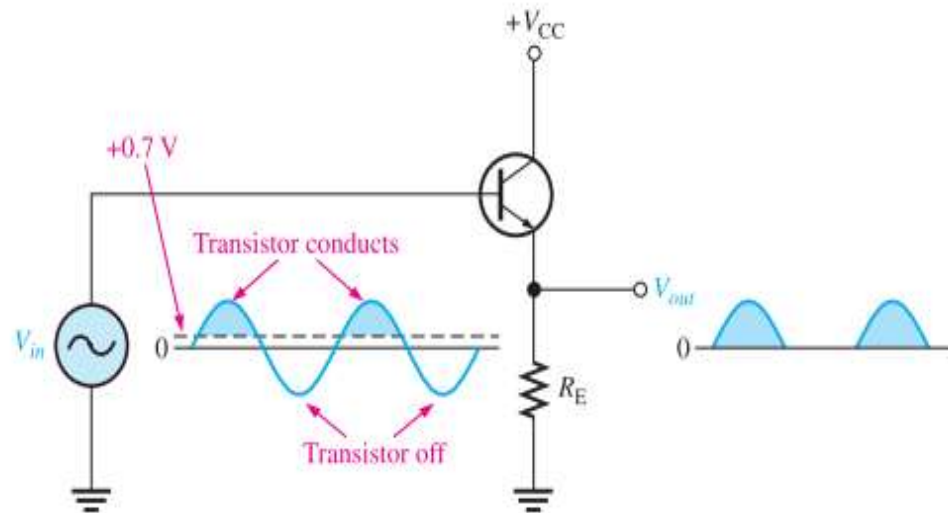- The Circuit only conducts for the positive half of the cycle.
- Can not amplify the entire cycle




emitter-follower circuit

## Class B Push-Pull Operation

- To amplify the entire cycle, it is necessary to add a second class B amplifier that operates on the negative half of the cycle.
- The combination of two class B amplifiers working together is called push-pull operation
- There are **two common approaches** for using push-pull amplifiers to reproduce the entire waveform.
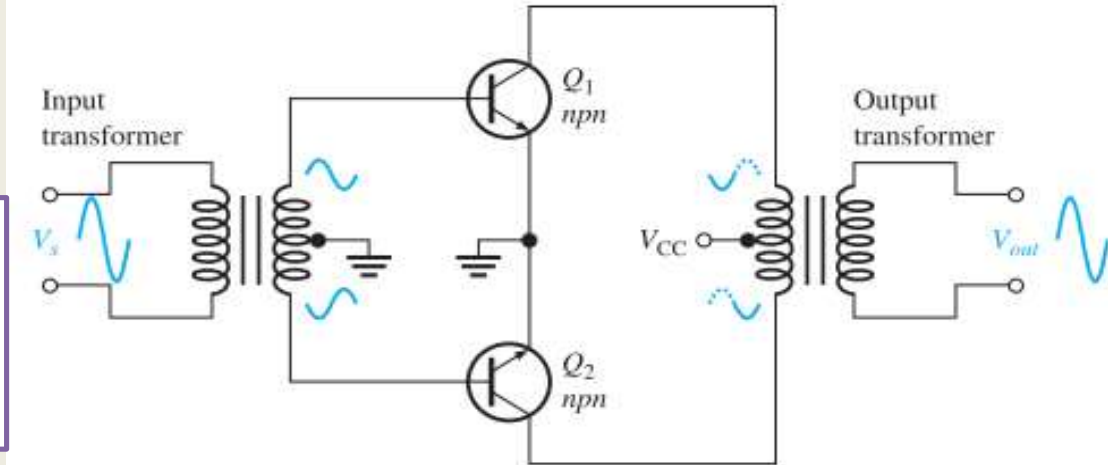
### 1. Transformer Coupling


- ✓ The input transformer thus converts the input signal to two out-of-phase signals for the two npn transistors.




- ✓ The output transformer combines the signals by permitting current in both directions, even though one transistor is always cut off.
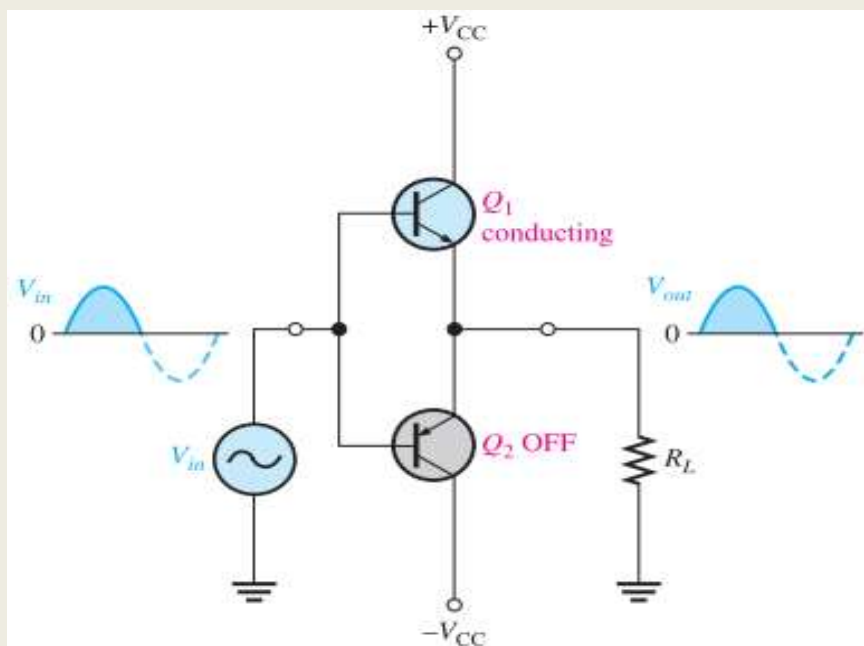
## 2. Complementary Symmetry Transistors

- ✓ The figure shows one of the most popular types of push-pull class B amplifiers using two emitter-followers and both positive and negative power supplies.
- ✓ This is a complementary amplifier because one emitter-follower uses an npn transistor and the other a pnp, which conduct on opposite alternations of the input cycle.




(a) During a positive half-cycle

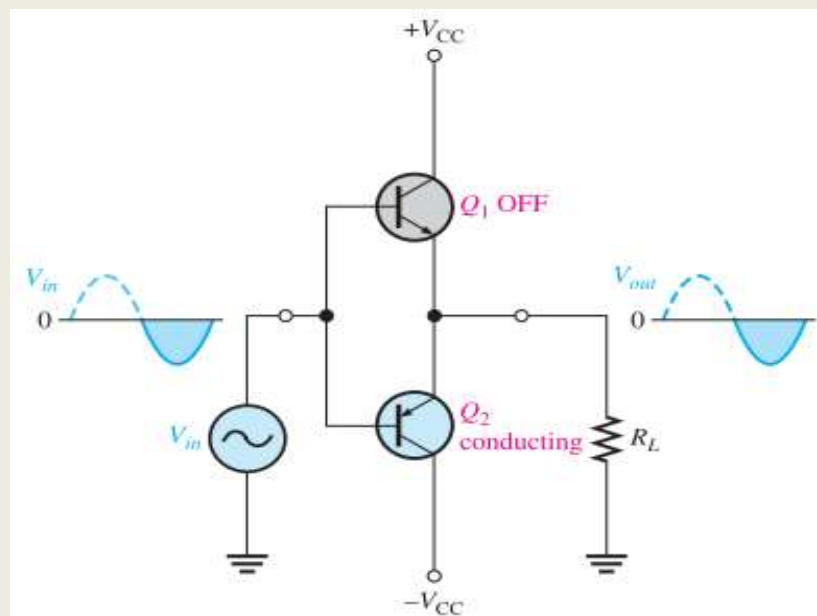

(b) During a negative half-cycle
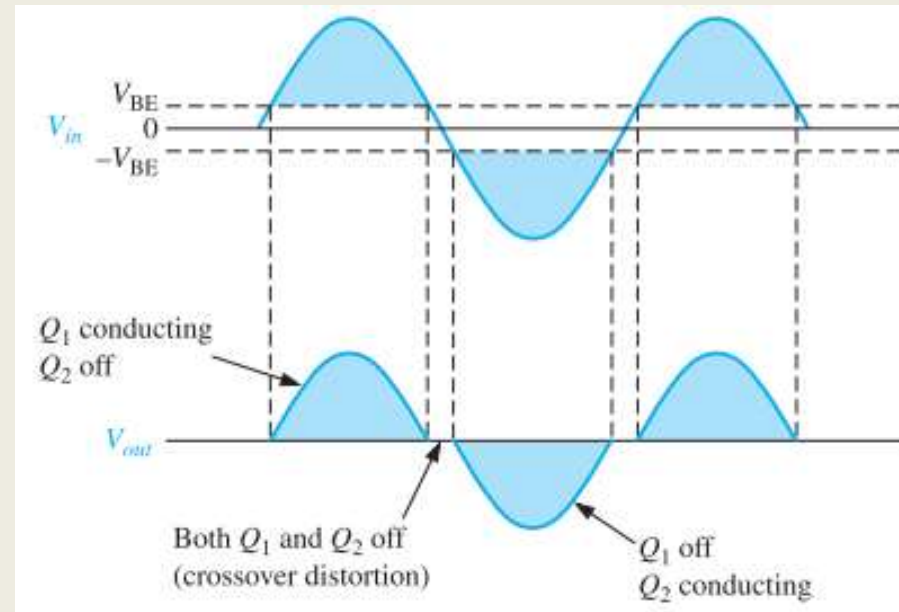
## Crossover Distortion

- ✓ When the dc base voltage is zero, both transistors are off and the input signal voltage must exceed  $V_{BE}$  before a transistor conducts.
- ✓ Because of this, there is a time interval between the positive and negative alternations of the input when neither transistor is conducting, as shown in Figure.
- ✓ The resulting distortion in the output waveform is called **crossover distortion**.



## Biasing the Push-Pull Amplifier for Class AB Operation


- ✓ To overcome crossover distortion, the biasing is adjusted to just overcome the VBE of the transistors
- ✓ In class AB operation, the push-pull stages are biased into slight conduction, even when no input signal is present.
- ✓ This can be done with a voltage-divider and diode arrangement, as shown

➤ Using equal values of  $R_1$  and  $R_2$  the positive and negative supply voltages forces the voltage at point A to equal 0 V and eliminates the need for an input coupling capacitor.

➤ When the diode characteristics of  $D_1$  and  $D_2$  are closely matched to the characteristics of the transistor BE junctions, the current in the diodes and the current in the transistors are the same;  
**((current mirror.))**

The diode current will be the same as  $I_{CQ}$

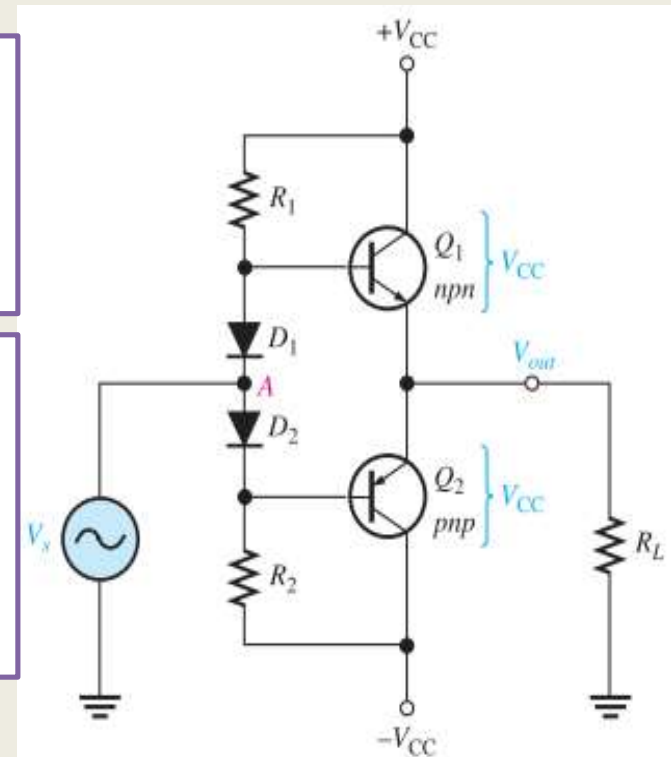
$$I_{CQ} = \frac{V_{CC} - 0.7 \text{ V}}{R_1}$$



## ✓ AC Operation

- The Q-point is slightly above cutoff. (In a true class B amplifier, the Q-point is at cutoff.)
- The ac cutoff voltage is at  $V_{CC}$
- The ac saturation current is:

$$I_{c(sat)} = \frac{V_{CC}}{R_L}$$

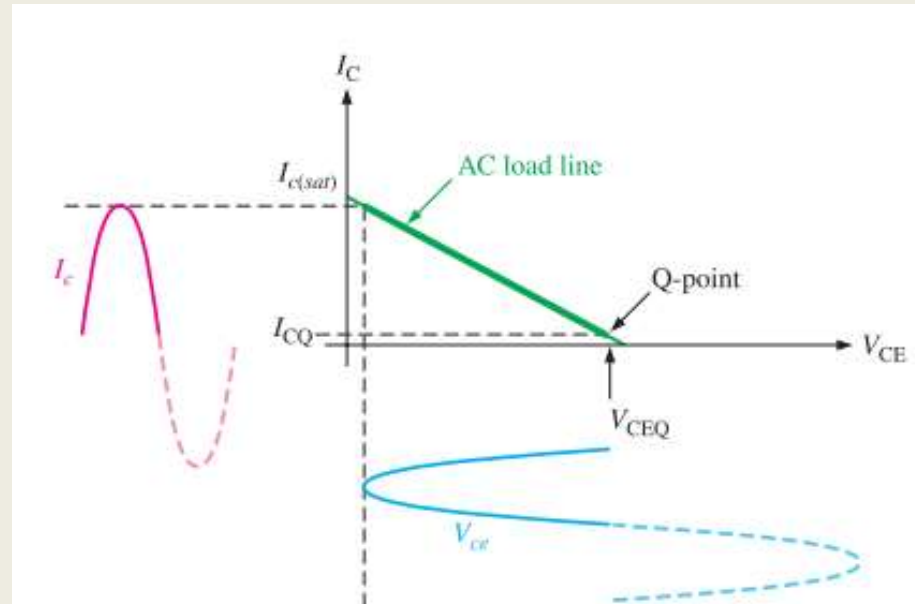

- ✓ In class A , the Q-point is near the middle and there is significant current in the transistors even with no signal.
- ✓ In class B , when there is no signal, the transistors have only a very small current and therefore dissipate very little power.
- ✓ Thus, the efficiency of a class B amplifier can be much higher than a class A amplifier.

The ideal maximum peak output voltage is

$$V_{out(peak)} \cong V_{CEQ} \cong V_{CC}$$

The ideal maximum peak current is

$$I_{out(peak)} \cong I_{c(sat)} \cong \frac{V_{CC}}{R_L}$$




## Single-Supply Push-Pull Amplifier

- The circuit operation is the same as that described previously, except the bias is set to force the output emitter voltage to be

$$V_{out(peak)} \cong V_{CEQ} = \frac{V_{CC}}{2}$$
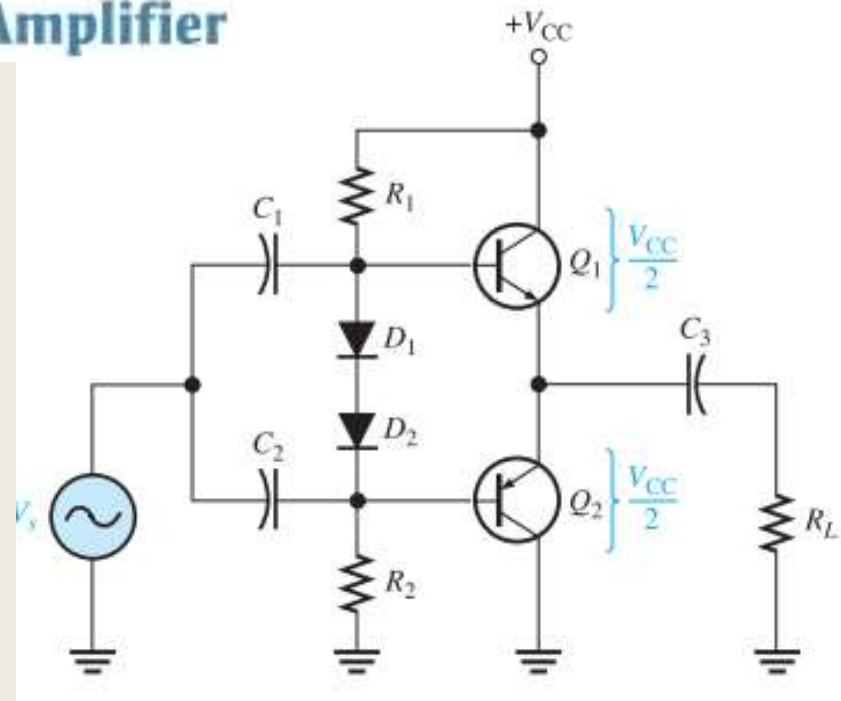
$$I_{out(peak)} \cong I_{c(sat)} = \frac{V_{CEQ}}{R_L}$$



## Maximum Output Power

$$P_{out} = I_{out(rms)} V_{out(rms)}$$

$$P_{out} = 0.5 I_{c(sat)} V_{CEQ}$$

$$I_{out(rms)} = 0.707 I_{out(peak)} = 0.707 I_{c(sat)}$$

$$V_{out(rms)} = 0.707 V_{out(peak)} = 0.707 V_{CEQ}$$

Substituting  $V_{CC}/2$  for  $V_{CEQ}$ , the maximum average output power is

$$P_{out} = 0.25 I_{c(sat)} V_{CC}$$

## DC Input Power

The dc input power comes from the  $V_{CC}$  supply and is

$$P_{DC} = I_{CC} V_{CC}$$

Since each transistor draws current for a half-cycle, the current is a half-wave signal with an average value of

$$I_{CC} = \frac{I_{c(sat)}}{\pi}$$

$$P_{DC} = \frac{I_{c(sat)} V_{CC}}{\pi}$$

## Efficiency


$$\eta = \frac{P_{out}}{P_{DC}}$$

$$\eta_{max} = \frac{P_{out}}{P_{DC}} = \frac{0.25 I_{c(sat)} V_{CC}}{I_{c(sat)} V_{CC} / \pi} = 0.25 \pi$$

$$\eta_{max} = 0.79$$
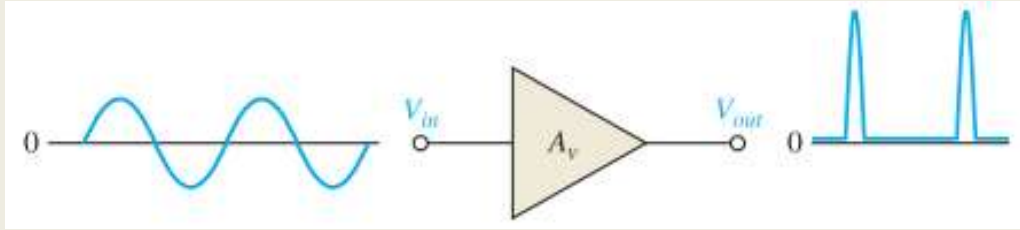
## Class C amplifiers


- Class C amplifiers are biased so that conduction occurs for much less than  $180^\circ$
- Class C amplifiers are more efficient than either class A, B, or AB



- The output amplitude is a nonlinear function of the input, so class C amplifiers are not used for linear amplification.
- They are generally used in radio frequency (RF) applications, including resonance circuits
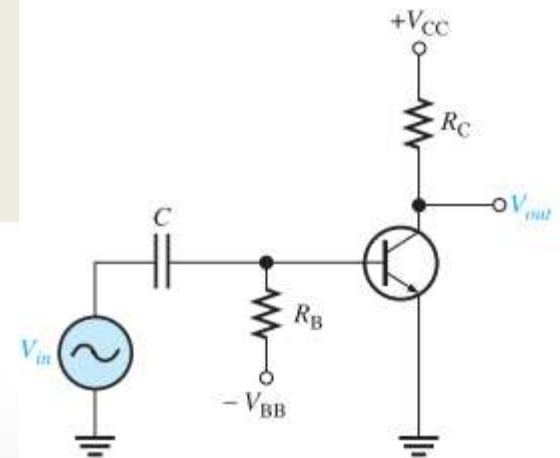
### Basic Class C Operation

- A class C amplifier is normally operated with a resonant circuit load, so the resistive load is used only for the purpose of illustrating the concept.
- The ac source voltage has a peak value that exceeds the barrier potential of the base-emitter junction for a short time near the positive peak of each cycle,



(a) Basic class C amplifier circuit

# Class C amplifiers

## Basic Class C Operation



- During this short interval, the transistor is turned on.
- The power dissipation of the transistor in a class C amplifier is low because it is on for only a small percentage of the input cycle
- The power dissipation during the on time is

$$P_{D(on)} = I_{C(sat)} V_{ce(sat)}$$

- The power dissipation averaged over the entire cycle is

$$P_{D(avg)} = \left( \frac{t_{on}}{T} \right) P_{D(on)} = \left( \frac{t_{on}}{T} \right) I_{C(sat)} V_{ce(sat)}$$

Check EXAMPLE 7–7 (Floyde)

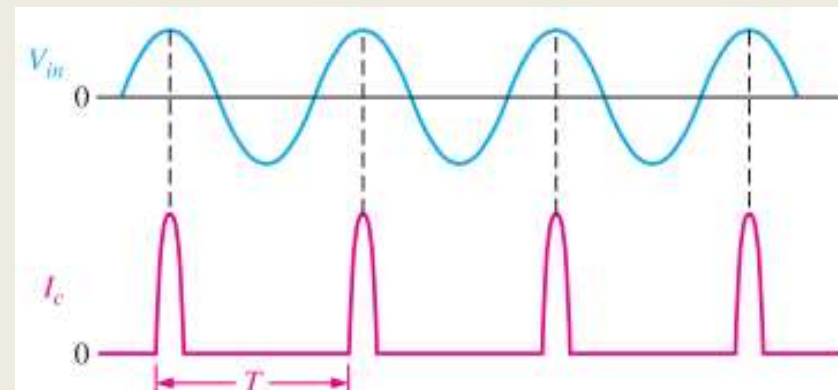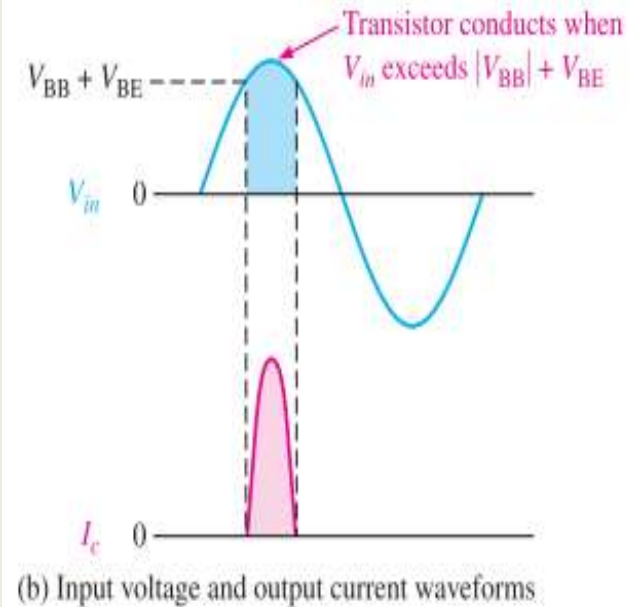

## Tuned Class C Operation

- Because the collector voltage (output) is not a replica of the input, the resistively loaded class C amplifier alone is of no value in linear applications.
  - It is therefore necessary to use a class C amplifier with a parallel resonant circuit (tank), as shown
- 
- The short pulse of collector current on each cycle of the input initiates and sustains the oscillation of the tank circuit so that an output sinusoidal voltage is produced

